

UC Berkeley
Teaching Professor
Dan Garcia

CS61C


Great Ideas
in
Computer Architecture
(a.k.a. Machine Structures)

RISC-V Processor Design
Control


Datapath Control

- We have designed a complete datapath
 - Capable of executing all RISC-V instructions in one cycle each
 - Not all units (hardware) used by all instructions
- 5 Phases of execution
 - IF, ID, EX, MEM, WB
 - Not all instructions are active in all phases
- Controller specifies how to execute instructions
 - We still need to design it


Our Single-Core Processor

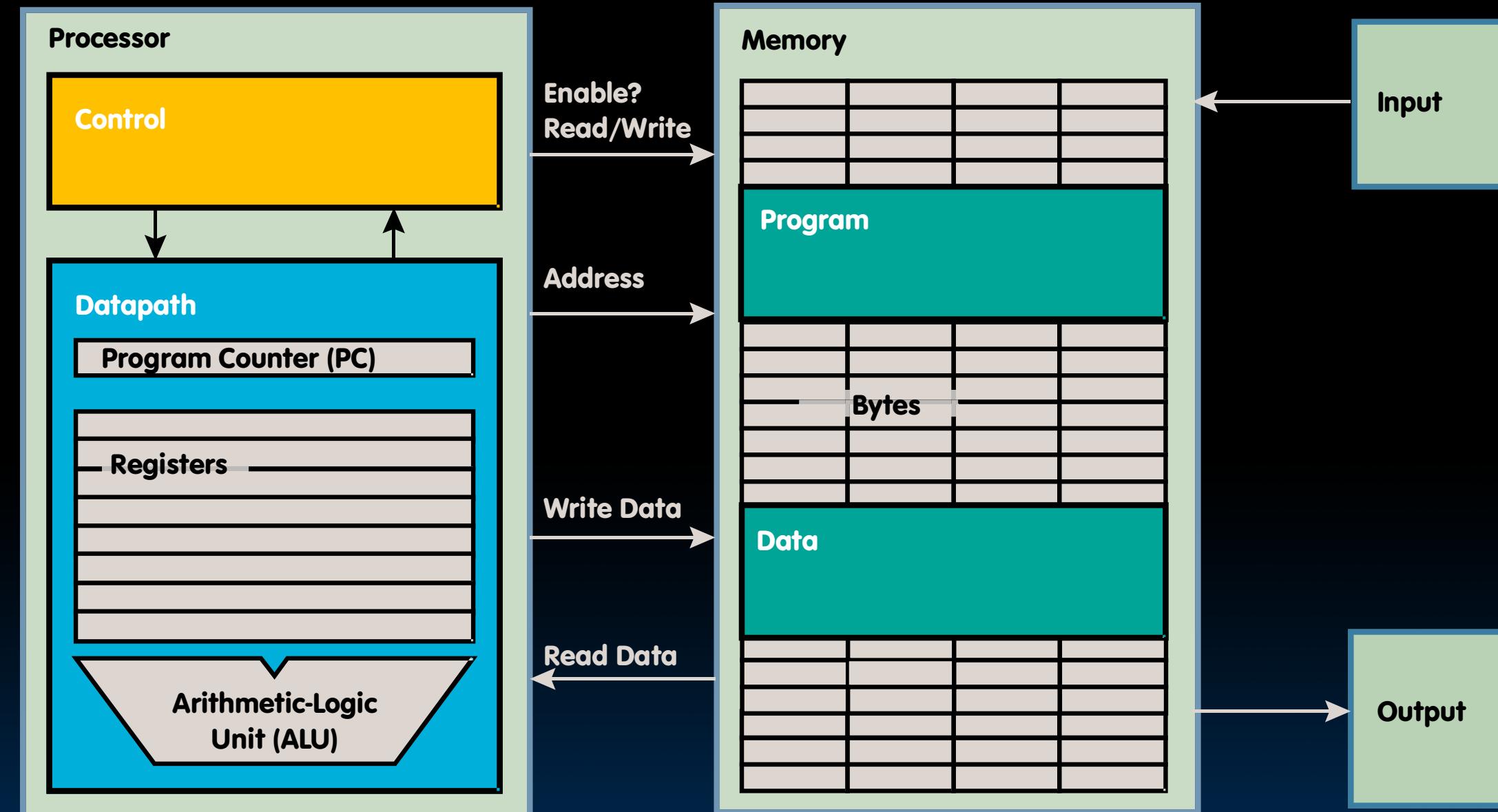


Single-Cycle RV32I Datapath and Control

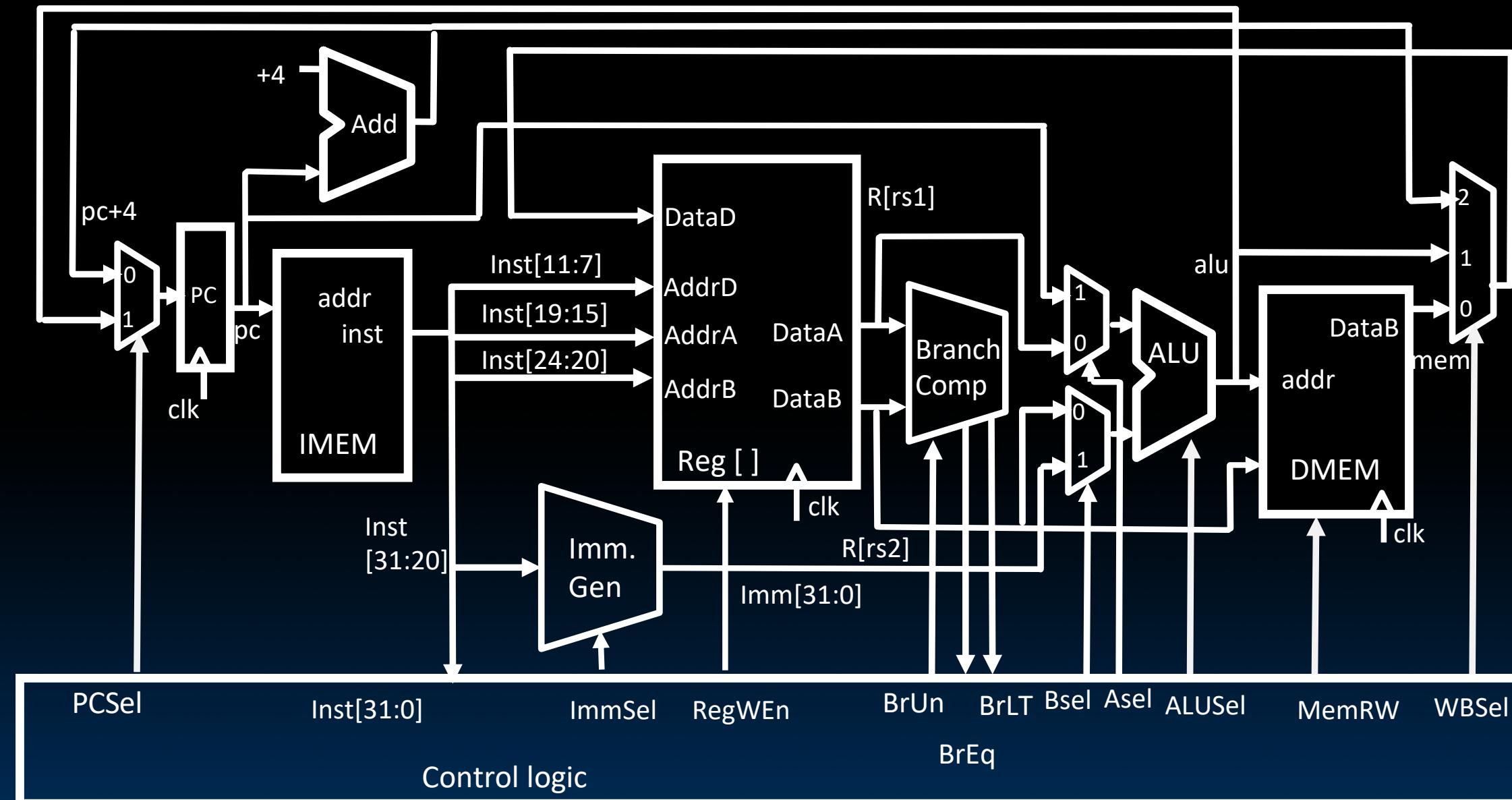

Example: sw reg, offset (regbaseptr)

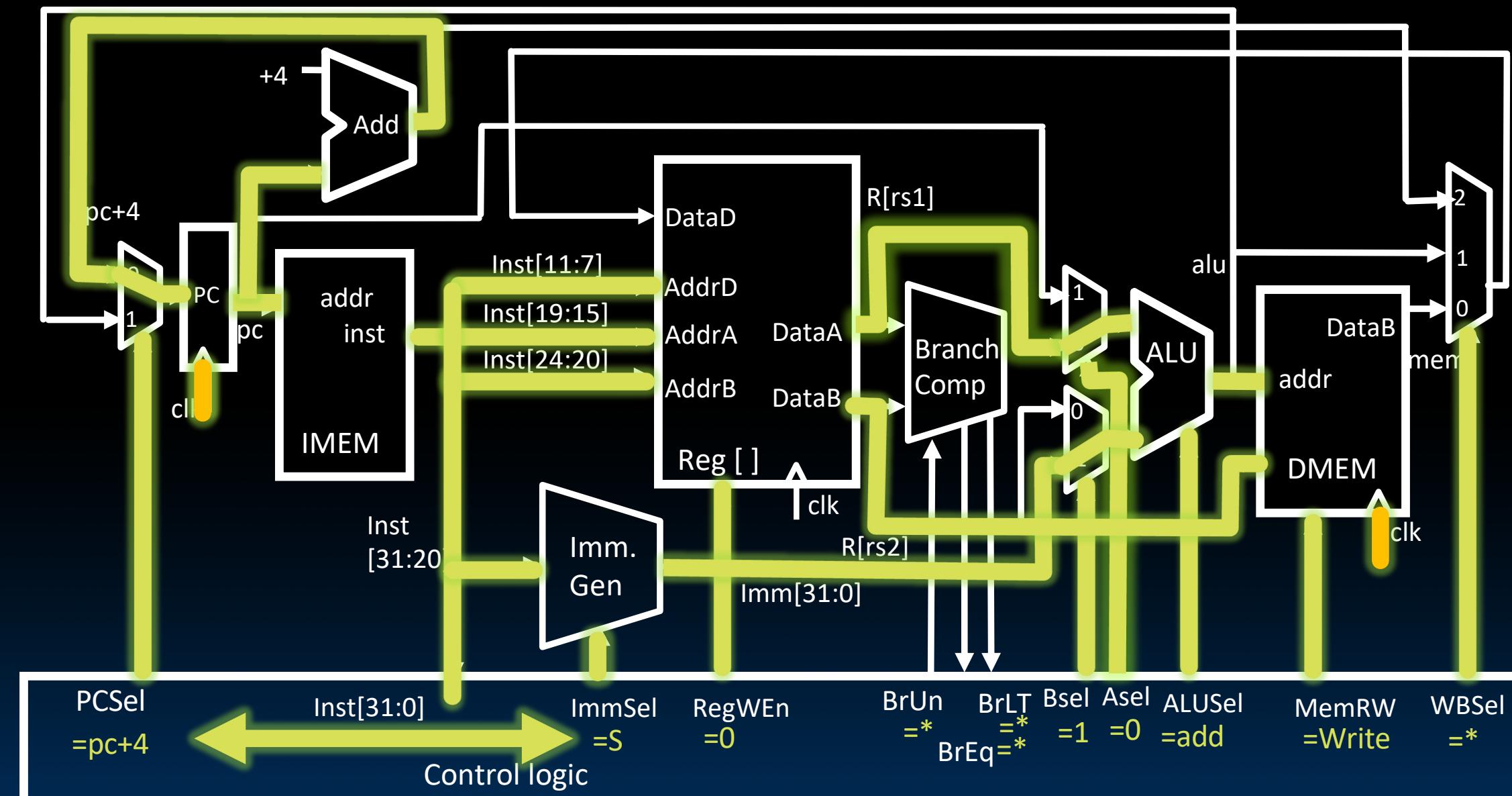


Example: beq reg1, reg2, Label

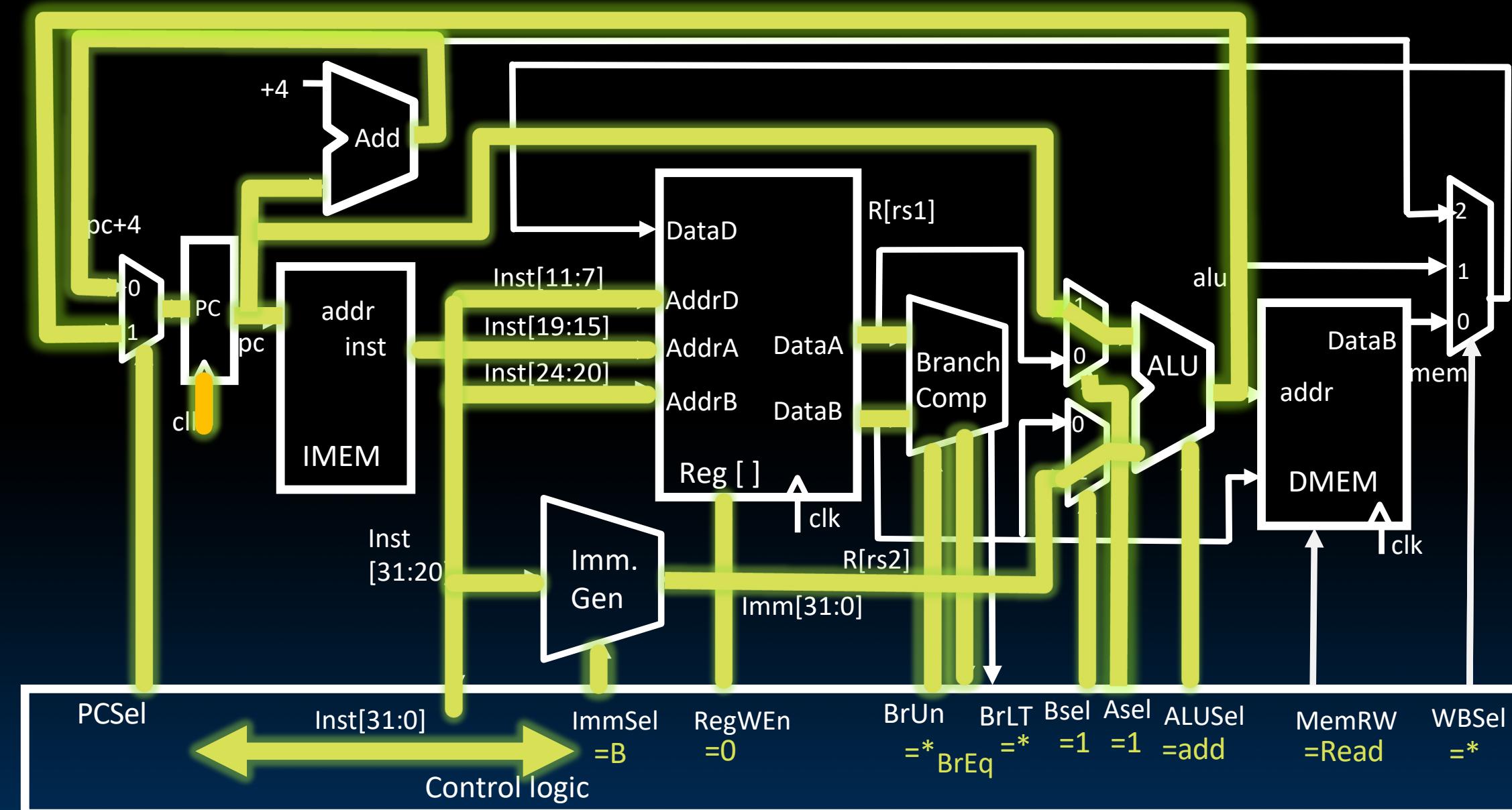



Instruction Timing

Example: add rd, reg1, reg2

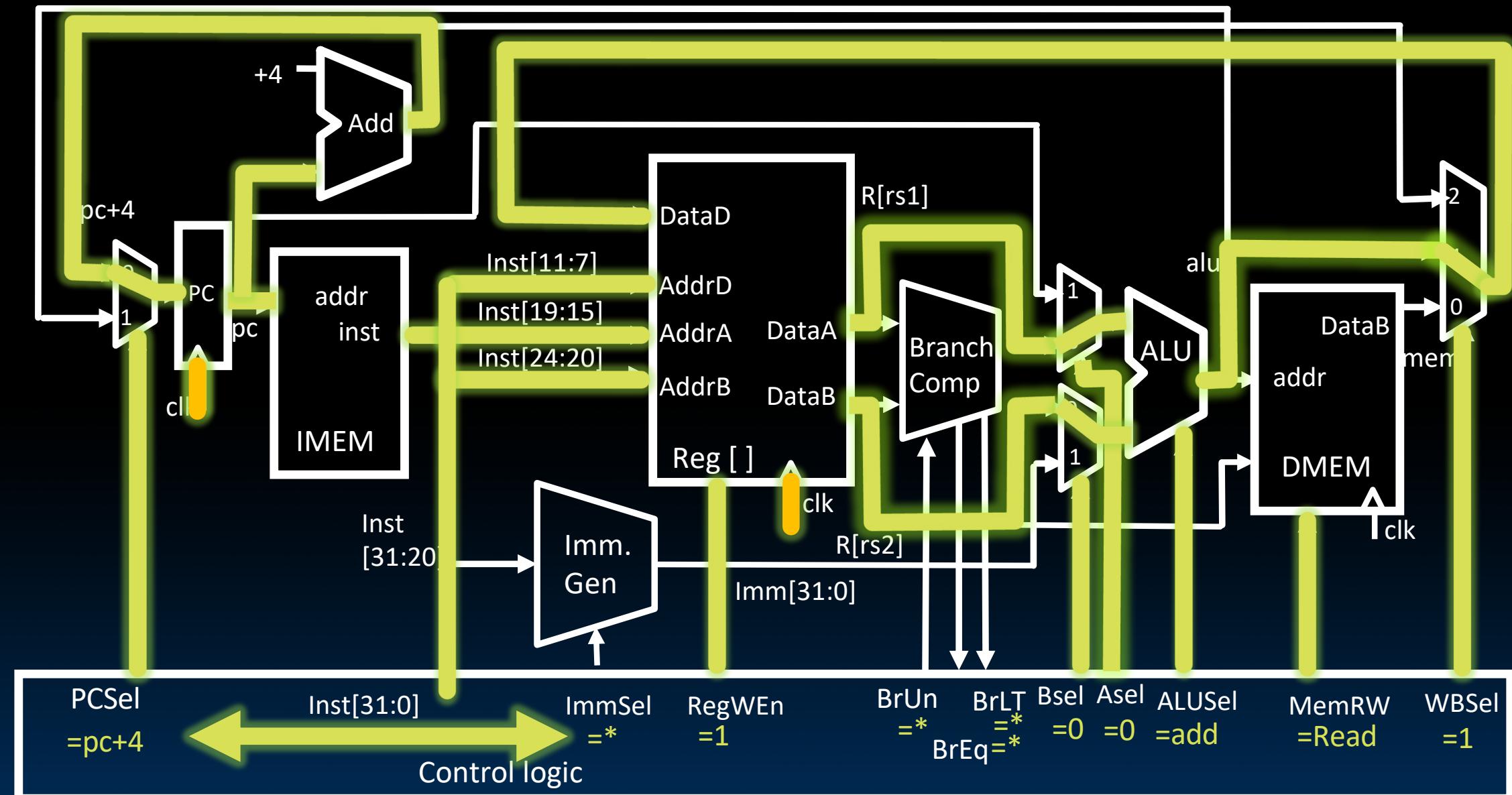


add Execution

e.g.,
add x1,x2,x3

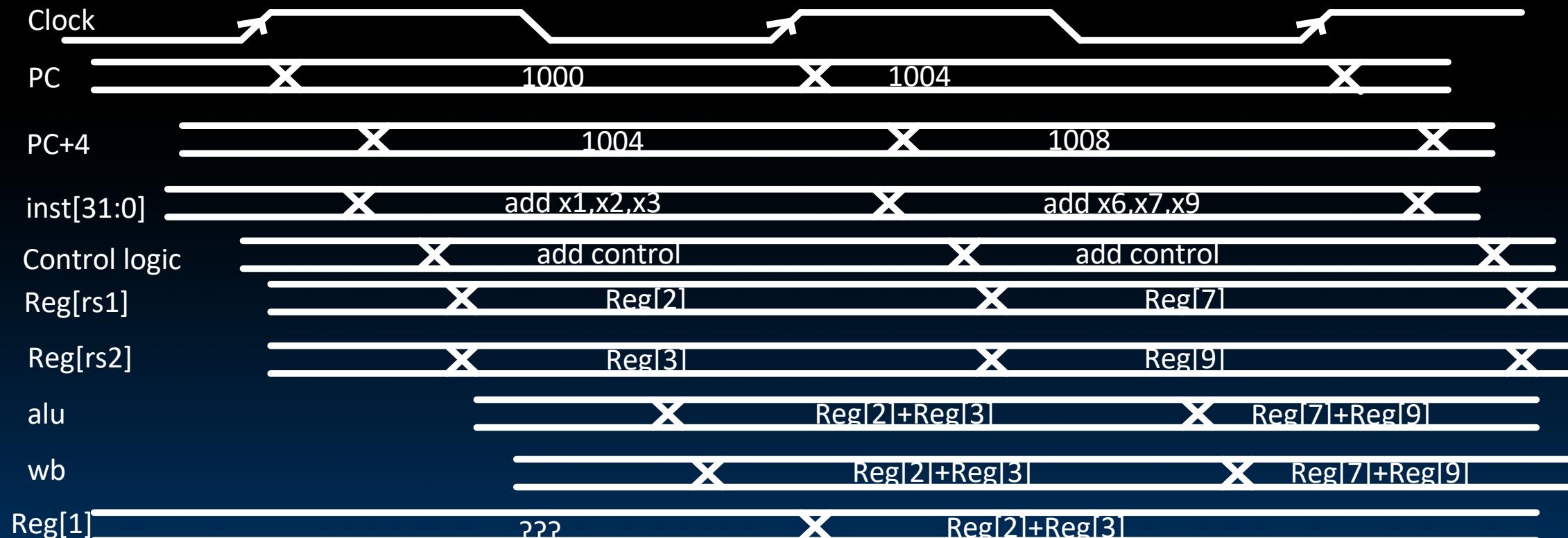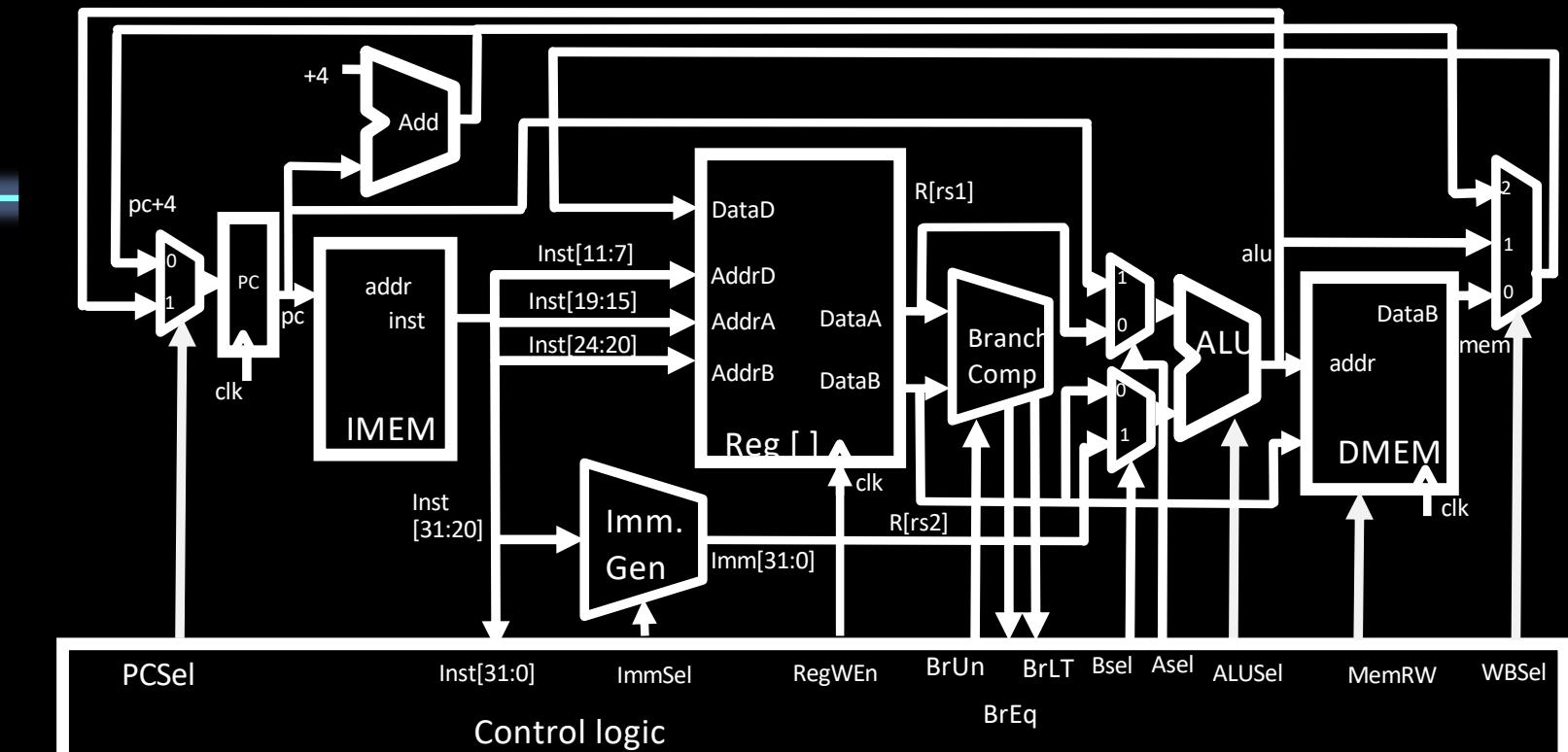


Example: add timing

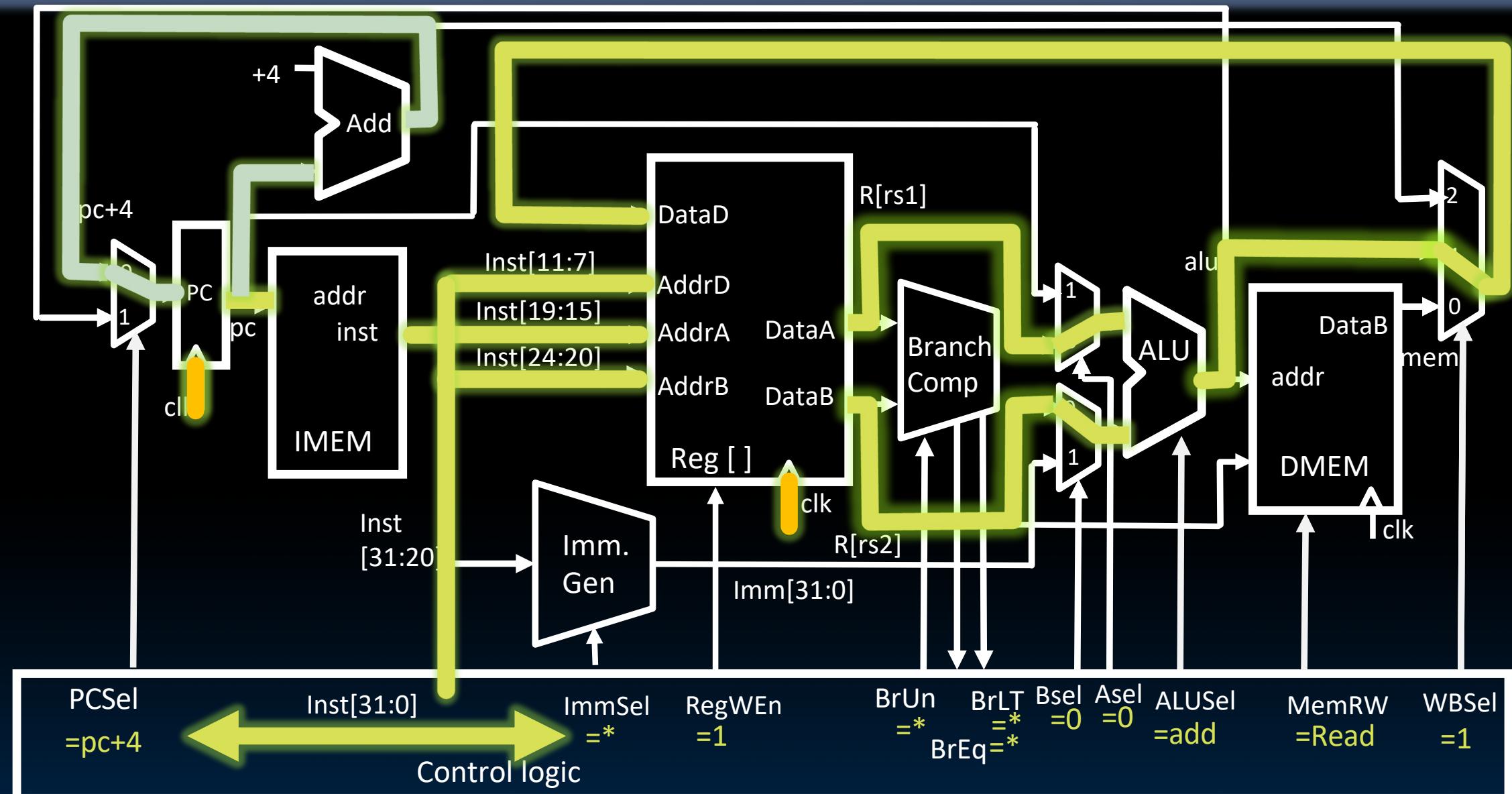


$$\begin{aligned}
 \text{Critical path} &= t_{\text{clk-q}} + \max \{ t_{\text{Add}} + t_{\text{mux}}, t_{\text{IMEM}} + t_{\text{Reg}} + t_{\text{mux}} + t_{\text{ALU}} + t_{\text{mux}} \} + t_{\text{setup}} \\
 &= t_{\text{clk-q}} + t_{\text{IMEM}} + t_{\text{Reg}} + t_{\text{mux}} + t_{\text{ALU}} + t_{\text{mux}} + t_{\text{setup}}
 \end{aligned}$$

Example: lw reg, offset (regbaseptr)

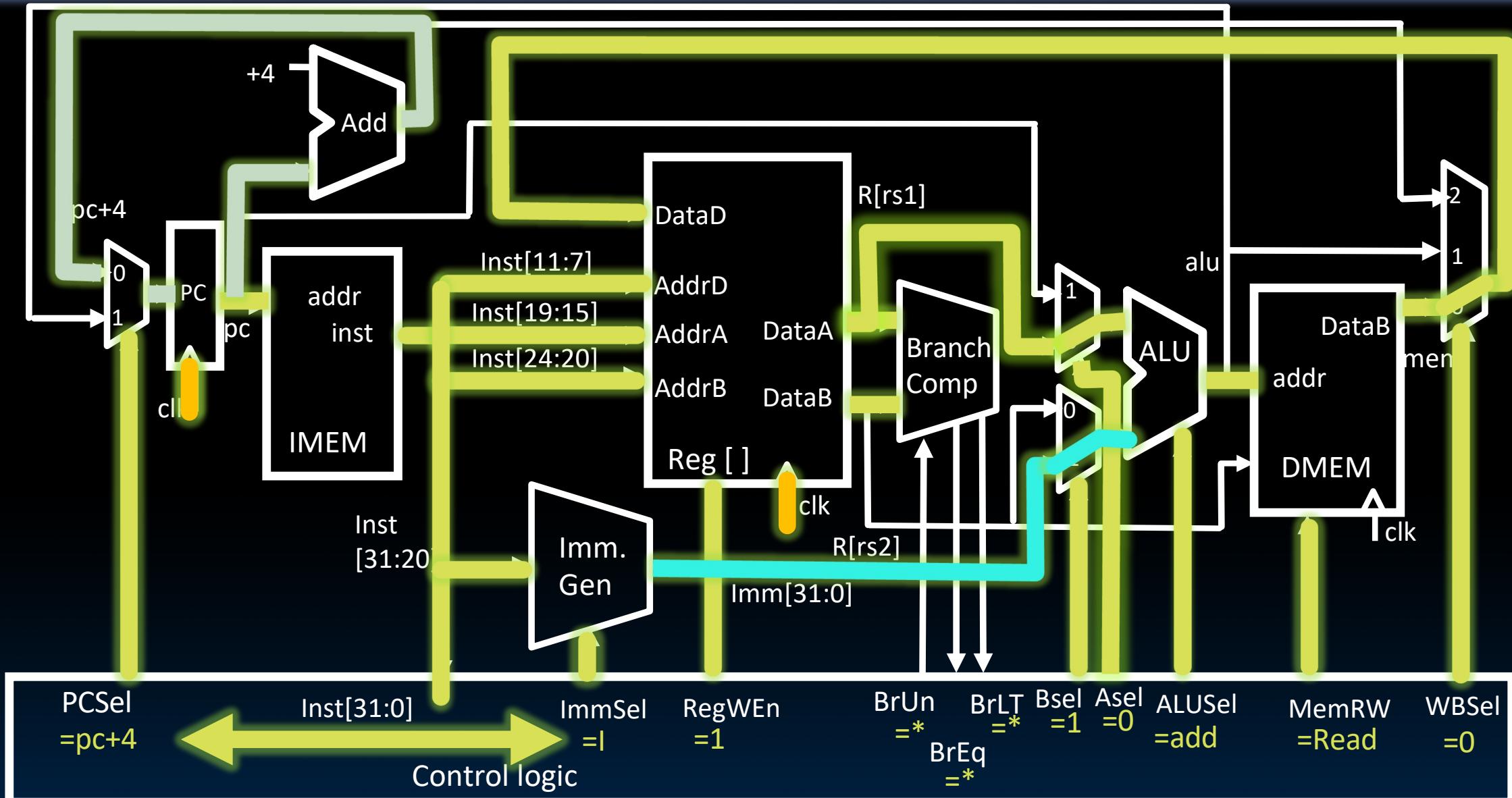

Critical path = $t_{clk-q} + \max \{ t_{Add} + t_{mux}, t_{IMEM} + t_{Imm} + t_{mux} + t_{ALU} + t_{DMEM} + t_{mux}, t_{IMEM} + t_{Reg} + t_{mux} + t_{ALU} + t_{DMEM} + t_{mux} \} + t_{setup}$

Instruction Timing

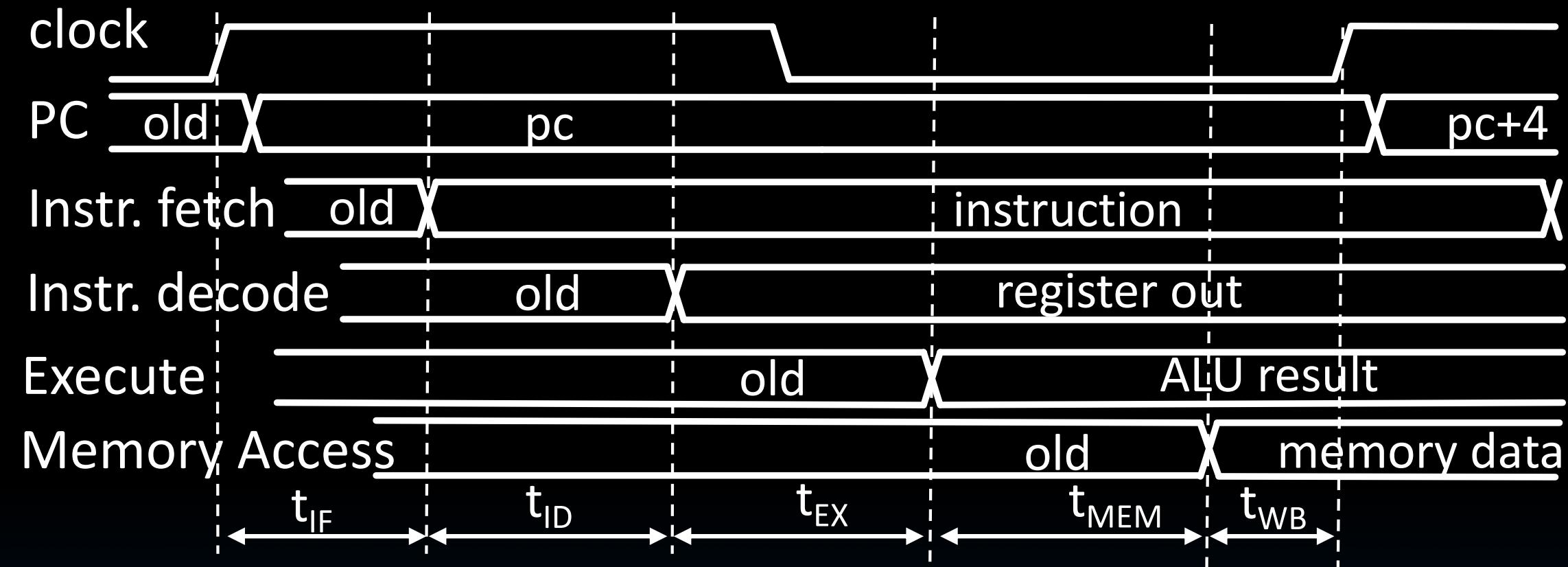

IF	ID	EX	MEM	WB	Total
I-MEM	Reg Read	ALU	D-MEM	Reg W	
200 ps	100 ps	200 ps	200 ps	100 ps	800 ps

Instruction Timing

Instr	IF = 200ps	ID = 100ps	ALU = 200ps	MEM=200ps	WB = 100ps	Total
add	X	X	X		X	600ps
beq	X	X	X			500ps
jal	X	X	X			500ps
lw	X	X	X	X	X	800ps
sw	X	X	X	X		700ps

- Maximum clock frequency
 - $f_{\max} = 1/800\text{ps} = 1.25 \text{ GHz}$
- Most blocks idle most of the time
 - E.g. $f_{\max, \text{ALU}} = 1/200\text{ps} = 5 \text{ GHz!}$

Control Logic Design

Control Logic Truth Table

Inst[31:0]	BrEq	BrLT	PCSel	ImmSel	BrUn	ASel	BSel	ALUSel	MemRW	RegWEn	WBSel
add	*	*	+4	*	*	Reg	Reg	Add	Read	1	ALU
sub	*	*	+4	*	*	Reg	Reg	Sub	Read	1	ALU
<i>(R-R Op)</i>	*	*	+4	*	*	Reg	Reg	(Op)	Read	1	ALU
addi	*	*	+4	I	*	Reg	Imm	Add	Read	1	ALU
lw	*	*	+4	I	*	Reg	Imm	Add	Read	1	Mem
sw	*	*	+4	S	*	Reg	Imm	Add	Write	0	*
beq	0	*	+4	B	*	PC	Imm	Add	Read	0	*
beq	1	*	ALU	B	*	PC	Imm	Add	Read	0	*
bne	0	*	ALU	B	*	PC	Imm	Add	Read	0	*
bne	1	*	+4	B	*	PC	Imm	Add	Read	0	*
blt	*	1	ALU	B	0	PC	Imm	Add	Read	0	*
bltu	*	1	ALU	B	1	PC	Imm	Add	Read	0	*
jalr	*	*	ALU	I	*	Reg	Imm	Add	Read	1	PC+4
jal	*	*	ALU	J	*	PC	Imm	Add	Read	1	PC+4
auipc	*	*	+4	U	*	PC	Imm	Add	Read	1	ALU

Control Realization Options

- ROM
 - “Read-Only Memory”
 - Regular structure
 - Can be easily reprogrammed
 - fix errors
 - add instructions
 - Popular when designing control logic manually
- Combinatorial Logic
 - Today, chip designers use logic synthesis tools to convert truth tables to networks of gates

RV32I, A Nine-Bit ISA!

imm[31:12]			rd	0110111	LUI
imm[31:12]			rd	0010111	AUIPC
imm[20:10:1111 19:12]			rd	1101111	JAL
imm[11:0]	rs1	000	rd	1100111	JALR
imm[12 10:5]	rs2	000	imm[4:1 11]	1100011	BEQ
imm[12 10:5]	rs2	001	imm[4:1 11]	1100011	BNE
imm[12 10:5]	rs2	100	imm[4:1 11]	1100011	BLT
imm[12 10:5]	rs2	101	imm[4:1 11]	1100011	BGE
imm[12 10:5]	rs2	110	imm[4:1 11]	1100011	BLTU
imm[12 10:5]	rs2	111	imm[4:1 11]	1100011	BGEU
imm[11:0]	rs1	000	rd	0000011	LB
imm[11:0]	rs1	001	rd	0000011	LH
imm[11:0]	rs1	010	rd	0000011	LW
imm[11:0]	rs1	100	rd	0000011	LBU
imm[11:0]	rs1	101	rd	0000011	LHU
imm[11:5]	rs2	000	imm[4:0]	0100011	SB
imm[11:5]	rs2	001	imm[4:0]	0100011	SH
imm[11:5]	rs2	010	imm[4:0]	0100011	SW
imm[11:0]	rs1	000	rd	0010011	ADDI
imm[11:0]	rs1	010	rd	0010011	SLTI
imm[11:0]	rs1	011	rd	0010011	SLTIU
imm[11:0]	rs1	100	rd	0010011	XORI
imm[11:0]	rs1	110	rd	0010011	ORI
imm[11:0]	rs1	111	rd	0010011	ANDI
0000000	shamt	001	rd	0010011	SLLI
0000000	shamt	101	rd	0010011	SRLI
0100000	shamt	101	rd	0010011	SRAI
0000000	rs2	000	rd	0110011	inst [6:2]
0100000	rs2	000	rd	0110011	inst [14:12]
0000000	rs2	001	rd	0110011	inst [30]
0000000	rs2	010	rd	0110011	ADD
0000000	rs2	011	rd	0110011	SUB
0000000	rs2	100	rd	0110011	SLL
0000000	rs2	101	rd	0110011	SLT
0000000	rs2	101	rd	0110011	SLTU
0000000	rs2	110	rd	0110011	XOR
0000000	rs2	111	rd	0110011	SRL
fm	pred	succ	rs1	000	SRA
00000000000000			00000	000	OR
00000000000001			00000	000	AND
					FENCE
					ECALL
					EBREAK

- Instruction type encoded using only 9 bits:
- inst [30], inst [14:12], inst [6:2]**

inst [6:2]

inst [14:12]

inst [30]

Combinational Logic Control


- Simplest example: BrUn

			inst[14:12]	inst[6:2]		
imm[12:10:5]	rs2	rs1	000	imm[4:1 11]	1100011	BEQ
imm[12:10:5]	rs2	rs1	001	imm[4:1 11]	1100011	BNE
imm[12:10:5]	rs2	rs1	100	imm[4:1 11]	1100011	BLT
imm[12:10:5]	rs2	rs1	101	imm[4:1 11]	1100011	BGE
imm[12:10:5]	rs2	rs1	110	imm[4:1 11]	1100011	BLTU
imm[12:10:5]	rs2	rs1	111	imm[4:1 11]	1100011	BGEU


- How to decode whether BrUn is 1?

$$\text{BrUn} = \text{inst}[13] \bullet \text{Branch}$$

ROM-based Control

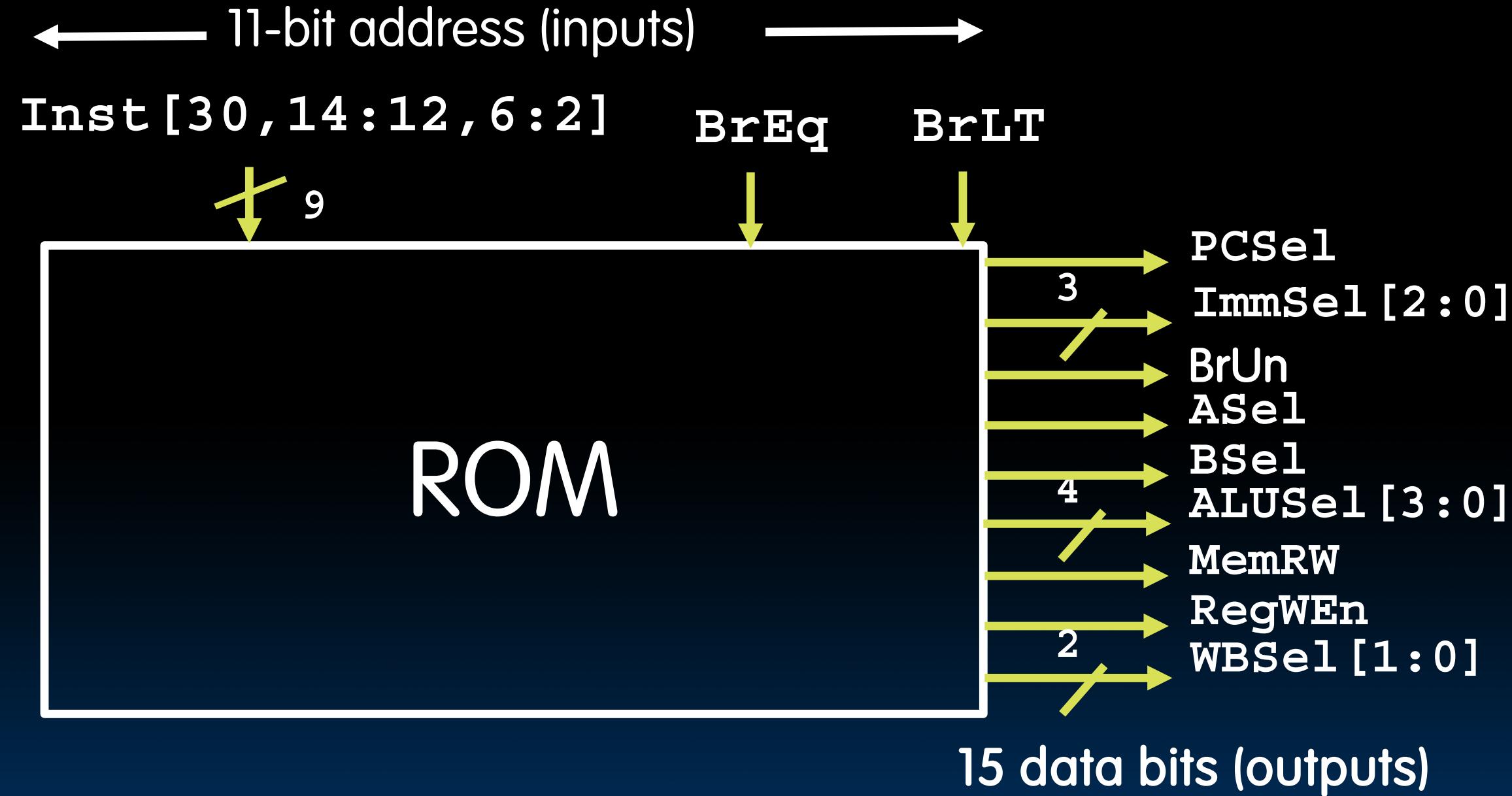

ROM Controller Implementation

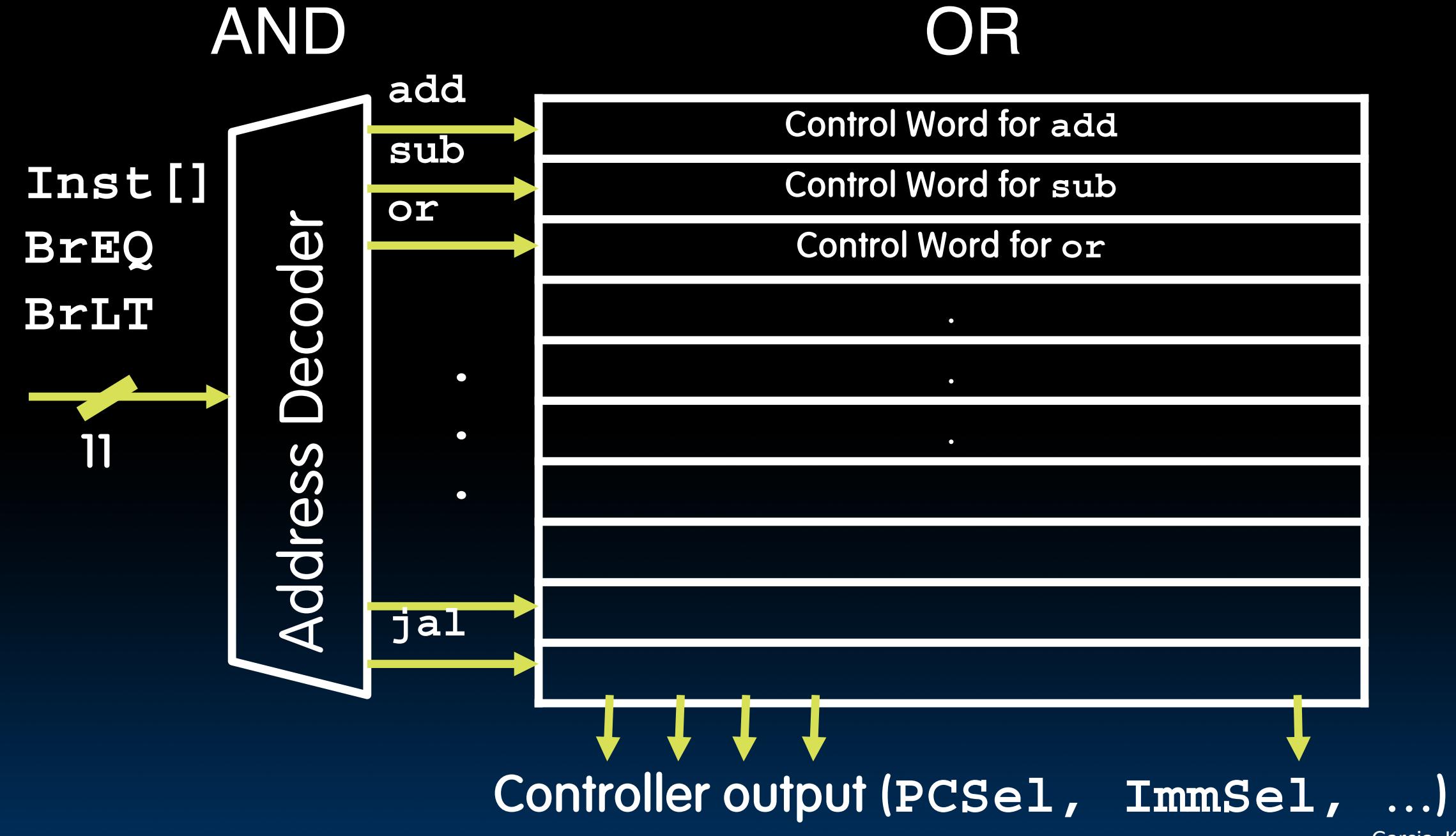

Control Logic to Decode add

inst [30]	inst [14:12]	inst [6:2]	
0000000	shamt	rs1	001 SLLI
0000000	shamt	rs1	101 SR LI
0100000	shamt	rs1	101 SRAI
0000000	rs2	rs1	000 ADD
0100000	rs2	rs1	000 SUB
0000000	rs2	rs1	001 SLL
0000000	rs2	rs1	010 SLT
0000000	rs2	rs1	011 SLTU
0000000	rs2	rs1	100 XOR
0000000	rs2	rs1	101 SRL
0100000	rs2	rs1	101 SRA
0000000	rs2	rs1	110 OR
0000000	rs2	rs1	111 AND

$$\text{add} = \overline{i[30]} \cdot \overline{i[14]} \cdot \overline{i[13]} \cdot \overline{i[12]} \cdot \text{R-type}$$

$$\text{R-type} = \overline{i[6]} \cdot i[5] \cdot i[4] \cdot \overline{i[3]} \cdot \overline{i[2]} \cdot \text{RV32I}$$

$$\text{RV32I} = i[1] \cdot i[0]$$

**“And In
Conclusion...”
(drum roll)**

Call home, we've made HW/SW contact!

High Level Language
Program (e.g., C)

| Compiler

Assembly Language
Program (e.g., RISC-V)

| Assembler

Machine Language
Program (RISC-V)

temp =
v[k] =
v[k+1]

lw x3, 0(x10)
lw x4, 4(x10)
sw x4, 0(x10)
sw x3, 4(x10)

1000 1101 1110 0010 0000 0000 0000 0000
1000 1110 0001 0000 00 0000 0000 0100
1010 1110 0001 0010 0000 0000 0000 0000
1010 1101 1110 0010 00 0000 0000 0100

Hardware Architecture Description
(e.g., block diagrams)

| Architecture Implementation

Logic Circuit Description
(Circuit Schematic Diagrams)



“And In conclusion...”

- We have built a processor!
 - Capable of executing all RISC-V instructions in one cycle each
 - Not all units (hardware) used by all instructions
 - Critical path changes
- 5 Phases of execution
 - IF, ID, EX, MEM, WB
 - Not all instructions are active in all phases
- Controller specifies how to execute instructions
 - Implemented as ROM or logic